

Registration No.:

--	--	--	--	--	--	--	--	--	--

Total Number of Pages: 02

Course: B.Tech/IDD
Sub_Code: EOPC2004

3rd Semester Regular Examination: 2024-25

SUBJECT: Digital Electronics

BRANCH(S): CST, CSEAIML, CSEDS, CSEAI, CSE, CSIT, CE, IT

Time: 3 Hours

Max Marks: 100

Q.Code: R500

Answer Question No.1 (Part-I) which is compulsory, any eight from Part-II and any two from Part-III.

The figures in the right hand margin indicate marks.

Part-I

Q1 Answer the following questions: (2 x 10)

- Find the hexadecimal number of $(243)_8$.
- Explain the role of transistors as switches in digital circuits.
- How many OR gate and half adder are required to implement a full adder Circuit?
- What is race around condition?
- What is essential prime implicant?
- What is the difference between combinational circuit and Sequential circuit?
- Design NAND gate and XOR gate using 2 - input NOR gate.
- What is a hazard in a combinational circuit?
- Convert the 100110 binary code into gray code.
- A 4 bit modulo-16 ripple counter uses JK flipflops. If the propagation delay of each Flipflop is 50 ns. Then find the maximum clock frequency.

Part-II

Q2 Only Focused-Short Answer Type Questions- (Answer Any Eight out of Twelve) (6 x 8)

- If $X = 111.101$ and $Y = 101.110$, Calculate $X + Y$, $X - Y$, and $Y - X$ by using 2's Complement method.
- Use the K-Map to simplify the expression $X = \bar{A} \cdot \bar{B} \bar{C} + \bar{B} C + \bar{A} B$.
- Implement the function $F = A(CD + B) + B\bar{C}$ using NAND gate only.
- Use the Quine-McCluskey technique to minimize the following Boolean function:
 $F(A, B, C) = \sum(1, 3, 5, 7)$
- Write short note on Mealey Morre Model of Finite State Machine.
- Design of NAND gate using CMOS.
- Explain the different types of Laws in Boolean function.
- Define and explain the operation of 4 bit shift register?
- Design a 3-bit binary counter using T flip flop.
- Design a Full adder circuit.

- k) Differentiate between decoder and demultiplexer. Under what circumstance a decoder can be converted into demultiplexer?
- l) Design and explain the Johnson Counter.

Part-III

Only Long Answer Type Questions (Answer Any Two out of Four)

- Q3** a) Design of 8×1 MUX using 2×1 MUX. (6+10)
b) Given that $f(A, B, C, D) = \sum(0, 1, 5, 7, 10, 14, 15)$. Implement this function using an appropriate Multiplexer.
- Q4** a) Derive the Characteristic Equation of D Flipflop. (6+10)
b) Convert the SR Flipflop to JK Flipflop.
- Q5** a) Minimize the Four variable logic function using K-Map. $f(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$ (8+8)
b) Design a simple logic circuit such that the outputs is 1 when the binary number A, B, C, D is greater than 0110.
- Q6** a) What are the salient features of an Algorithmic State Machine (ASM) chart? (6+10)
b) Design an ASM chart for a simple weighing machine.